

Microwave Engineering

HW-01a Solutions (10 points each)

1. Express $\frac{2+j6}{3-j4}$ in the polar coordinates.

(Answer) Use the Android program 'PowerCalc'.


$$\frac{2+j6}{3-j4} = 1.26e^{j124.7^\circ}$$

2. For express $\sqrt{\frac{2+j6}{3-j4}}$ in the polar coordinates.


(Answer) Use the Android program 'PowerCalc'.

$$\sqrt{\frac{2+j6}{3-j4}} = 1.12e^{j62.3^\circ}$$

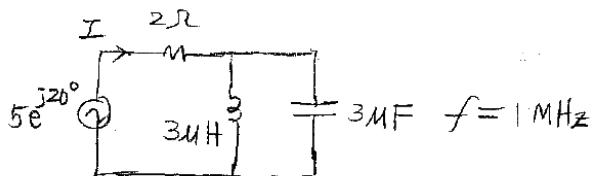3. Find the current I in the following circuit.



(Answer)

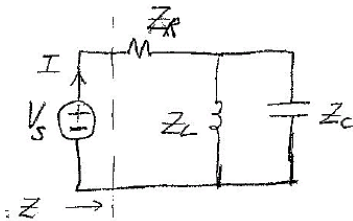


$$Z = Z_R + \frac{Z_L Z_C}{Z_L + Z_C}, Z_R = 2, Z_L = j\omega L = j18.8, Z_C = -j0.053$$

$$Z = 2 + \frac{18.8 \times 0.053}{j18.8 - j0.053} = 2 - j0.053 = 2e^{-j1.5^\circ}$$

$$I = \frac{V}{Z} = \frac{5e^{j20^\circ}}{2e^{-j1.5^\circ}} = 2.5e^{j21.5^\circ}$$

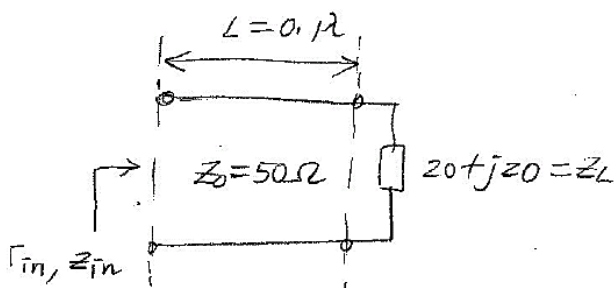4. Find the input impedance Z_{in} in the following circuit.



(Answer)

Method 1:

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta L}{Z_0 + jZ_L \tan \beta L} = 50 \frac{20 + j20 + j50 \tan((2\pi/\lambda)0.1\lambda)}{50 + (20 + j20)j50 \tan((2\pi/\lambda)0.1\lambda)} = 52.0 + j58.1 (\Omega)$$


Method 2:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{20 + j20 - 50}{20 + j20 + 50} = 0.495 e^{j130.4^\circ}$$

$$\Gamma_{in} = \Gamma_L e^{-j2\beta L} = 0.495 e^{j130.4^\circ} e^{-j2(2\pi/\lambda)(0.1\lambda)} = 0.495 e^{j58.4^\circ}$$

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.495 e^{j58.4^\circ}}{1 - 0.495 e^{j58.4^\circ}} = 52.0 + j58.0 (\Omega)$$

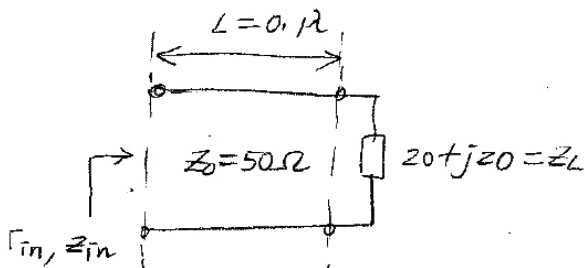5. Find the input reflection coefficient Γ_{in} in the following circuit.



(Answer)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{20 + j20 - 50}{20 + j20 + 50} = 0.495 e^{j130.4^\circ}$$

$$\Gamma_{in} = \Gamma_L e^{-j2\beta L} = 0.495 e^{j130.4^\circ} e^{-j2(2\pi/\lambda)(0.1\lambda)} = 0.495 e^{j58.4^\circ}$$