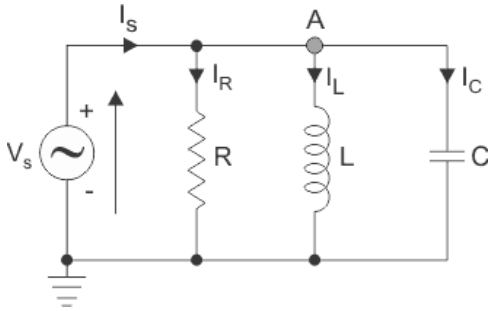


Microwave Engineering
HW01b Solutions (10 points each)

2.1




$$f = 1\text{MHz}, V_s = 5e^{j40^\circ}, R = 5\ \Omega, L = 1\mu\text{H}, C = 30\ \text{nF}$$

$$\omega L = 6.3\ \Omega, \frac{1}{\omega C} = 5.3\ \Omega$$

$$I_s = I_R + I_L + I_C = \frac{V_g}{R} + \frac{V_g}{j\omega L} + \frac{V_g}{1/j\omega C} = 5e^{j40^\circ} \left(\frac{1}{5} + \frac{1}{j6.3} + \frac{1}{-j5.3} \right) = 0.67 + j0.76 = 1.0 e^{j48.5^\circ} \text{ (A)}$$

2.2

characteristic impedance of a coax.

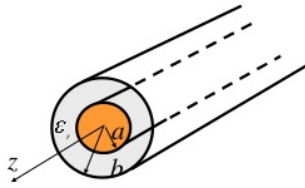

$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln\left(\frac{b}{a}\right)} \text{ F/m}$$

$$L = \frac{\mu_0}{2\pi} \ln\left(\frac{b}{a}\right) \text{ H/m}$$


$$Z_0 = \frac{1}{2\pi} \sqrt{\frac{\mu_0}{\epsilon_0}} \frac{1}{\sqrt{\epsilon_r}} \ln\left(\frac{b}{a}\right)$$

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\frac{\mu_0}{2\pi} \ln\left(\frac{b}{a}\right)}{\frac{2\pi\epsilon_0\epsilon_r}{\ln\left(\frac{b}{a}\right)}}}$$

$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \frac{b}{a}$$

$$a = 1.5, b = 4.5, \epsilon_r = 2.1 \rightarrow Z_0 = \frac{60}{\sqrt{2.1}} \ln \frac{4.5}{1.5} = 45.5\ \Omega$$

2,3

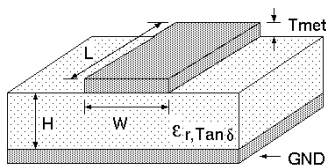

Use an online program: <http://www.emtalk.com/mscalc.php>

$$H = 1\ \text{mm}, W = 2\ \text{mm}, \epsilon_r = 4.3$$

$$Z_0 = 49.4\ \Omega$$