

Lecture 4 Impedance Matching (1)

1. What is the Impedance Matching?
2. Maximum Power Transfer Theorem
3. Reflectionless Matching
4. Conjugate Matching
5. Impedance Matching of Two-port Networks
6. Coding Example

1. What is the Impedance Matching?

■ Impedance matching

- To deliver the maximum power to a load from a source
- The source impedance has a specified value.
- The load impedance can be varying.
- Find a network that transforms the load impedance for maximum power transfer from the source to the load.

■ Applications

- Antennas and receiver front-ends
- Amplifiers
- Sensors and transducer



■ Related topics

- Network synthesis

2. Maximum Power Transfer Theorem

- Maximum power transfer for DC circuits

$$\eta = \frac{R_L}{R_S + R_L}$$

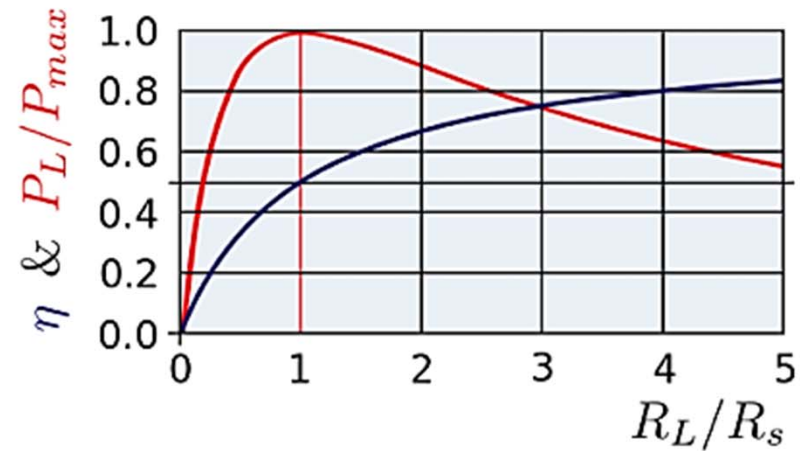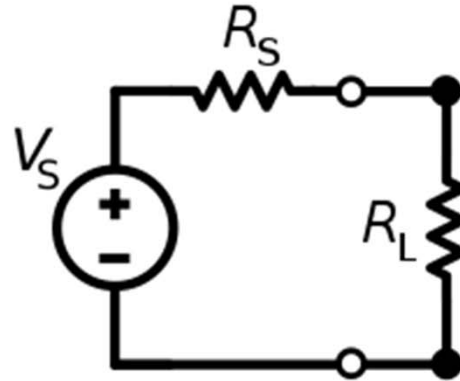


$$P_L = I^2 R_L = \left(\frac{V_S}{R_S + R_L} \right)^2 R_L = \frac{R_L}{(R_S + R_L)^2} V_S^2$$

$$\frac{\partial P_L}{\partial R_L} = 0 \rightarrow \boxed{R_L = R_S}$$

$$P_L = P_{L,\max} = \frac{V_S^2}{4R_S} = \frac{1}{2} P_S = \frac{1}{2} V_S I$$

$$P_S = P_{R_S} + P_{R_L} = 2P_L$$

- Maximum power transfer for AC networks

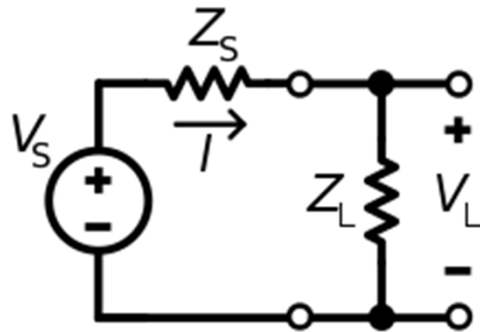

$$P_L = \text{Re}(V_L I^*) = \text{Re} \left[\frac{Z_L}{Z_S + Z_L} V_S \frac{1}{(Z_S + Z_L)^*} V_S^* \right] = \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} |V_S|^2$$


$$\frac{\partial P_L}{\partial R_L} = 0 \quad \text{and} \quad \frac{\partial P_L}{\partial X_L} = 0 \rightarrow \boxed{R_L = R_S \quad \text{and} \quad X_L = -X_S}$$

$$Z_L = Z_S^*$$

$$P_L = P_{L,\max} = \frac{1}{2} \frac{R_L}{(R_S + R_L)^2} |V_S|^2 = \frac{1}{2} P_S$$

3. Scattering Parameters

- Scattering parameter, S-parameter

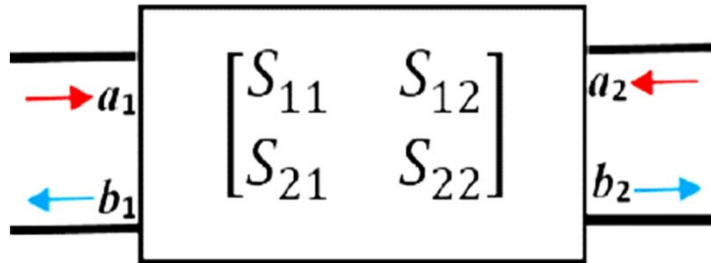

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

$$a_n = \frac{V_{0n}^+}{\sqrt{Z_{0n}}} : \text{incident wave at port } n$$

$$b_n = \frac{V_{0n}^-}{\sqrt{Z_{0n}}} : \text{reflected wave at port } n$$

$$S_{mn} = \frac{b_m}{a_n} = \frac{V_{0m}^-}{V_{0n}^+} \frac{\sqrt{Z_{0n}}}{\sqrt{Z_{0m}}} \quad (a_k = 0 \text{ for all } k \neq n) : \text{scattering parameter}$$

- Power at port n

$$P_n^+ = \frac{|V_{0n}^+|^2}{2Z_{0n}} = \frac{|a_n|^2}{2} : \text{incident power at port } n$$

$$P_n^- = \frac{|V_{0n}^-|^2}{2Z_{0n}} = \frac{|b_n|^2}{2} : \text{reflected power at port } n$$

$$P_n = P_n^+ - P_n^- : \text{power delivered to port } n$$

- Lossless network: unitary condition

$$\sum_{k=1}^N |S_{nk}|^2 = 1 \quad \text{for } n = 1, \dots, N \quad (\text{power conservation law})$$


- Reciprocal network:

$$S_{mn} = S_{nm}$$

■ Scattering parameters of simple networks


- Transmission line
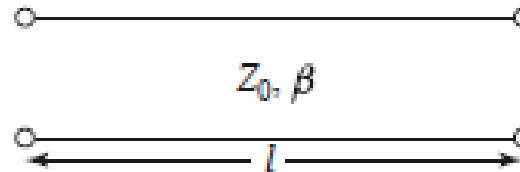
$$[S] = \begin{bmatrix} 0 & e^{-j\beta\ell} \\ e^{-j\beta\ell} & 0 \end{bmatrix}$$




- Series element on transmission line
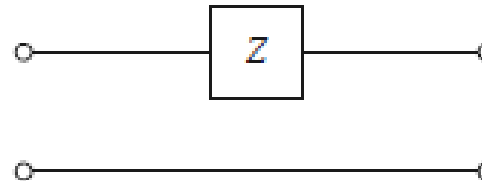
$$[S] = \begin{bmatrix} \frac{Z}{2Z_0 + Z} & \frac{Z_0 + Z}{2Z_0 + Z} \\ \frac{Z_0 + Z}{2Z_0 + Z} & \frac{Z}{2Z_0 + Z} \end{bmatrix}$$



- Shunt element on transmission line

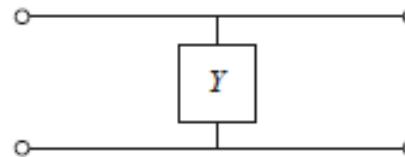
$$[S] = \begin{bmatrix} \frac{-Y}{2Y_0 + Y} & \frac{2Y_0}{2Y_0 + Y} \\ \frac{2Y_0}{2Y_0 + Y} & \frac{-Y}{2Y_0 + Y} \end{bmatrix}$$



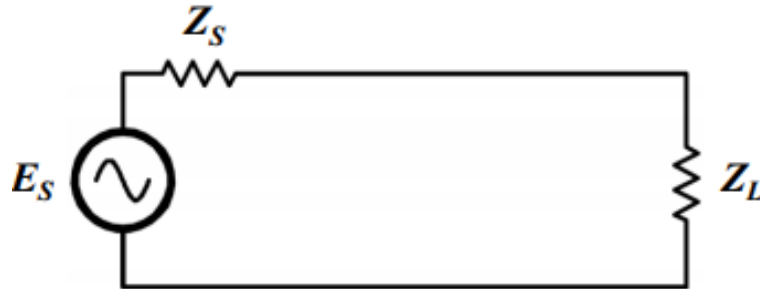4. Conjugate Matching


- Maximum power transfer theorem for two-ports

- S. D. Stearns, ARRL Pacificon Antenna Seminar, 2011



Source
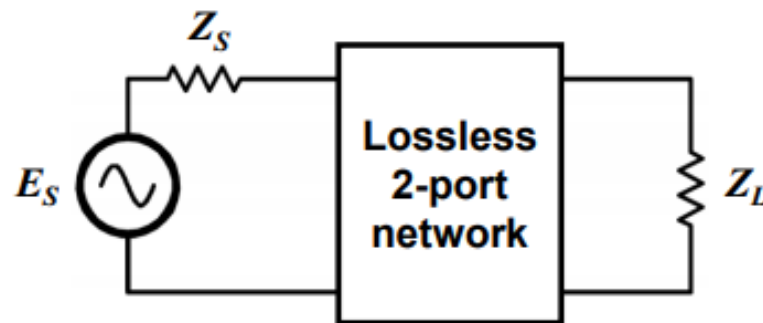
$$Z_L = Z_s^* \text{ (conjugate matching)}$$




Source



$$Z_{\text{in}} = Z_s^* \Leftrightarrow Z_{\text{out}} = Z_L^* \text{ (simultaneous conjugate matching)}$$

- Two-port matching network design [www.ittc.ku.edu/~jstiles/723/]
 - Find the equivalent circuit at the output of the two-port network using the open-circuit and short-circuit method.
 - Design a two-port network for the conjugate matching at the load.

$$Z_{\text{out}} = Z_L^*$$

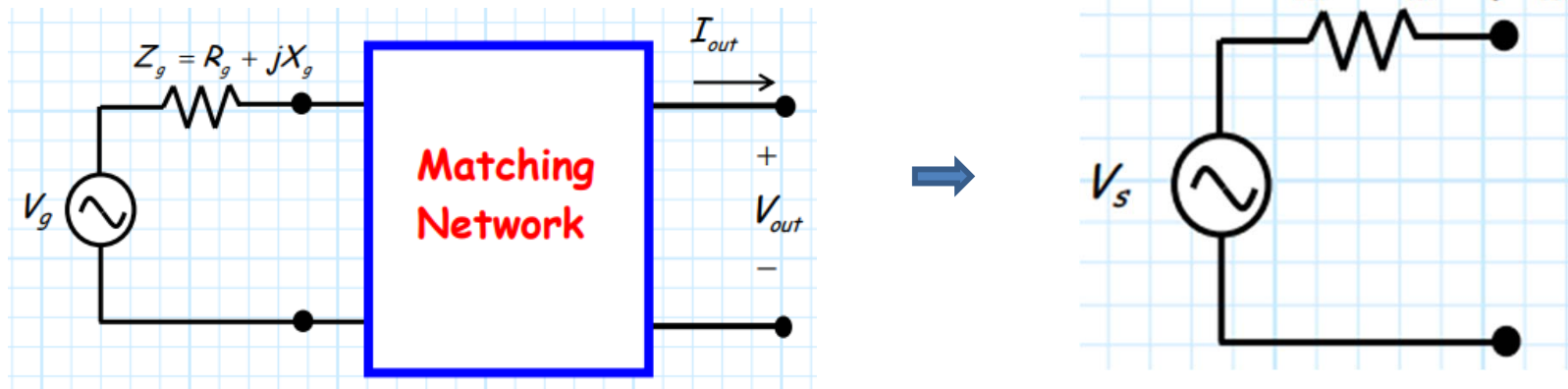

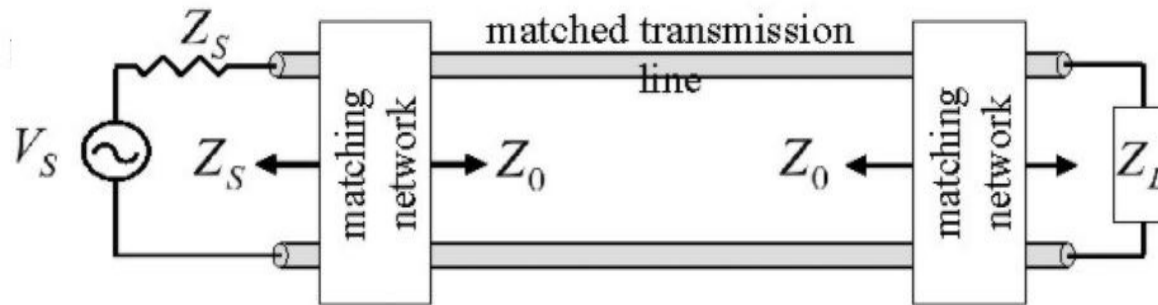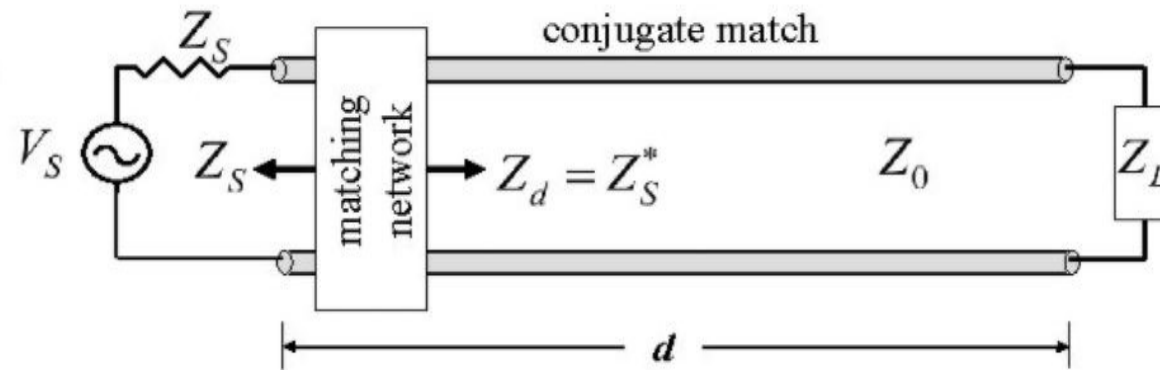- Source-load connected with a transmission line




$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = 0 \rightarrow \boxed{Z_L = Z_0}$$

- Case 1: Load not matched to Z_0 and input conjugate-matched $\rightarrow$ standing wave and additional loss with standing wave
- Case 2: Load matched to Z_0 and input matched to $Z_0 \rightarrow$ VSWR = 1 and no additional loss

5. Impedance Matching of Two-port Networks

- Two-port network power gains

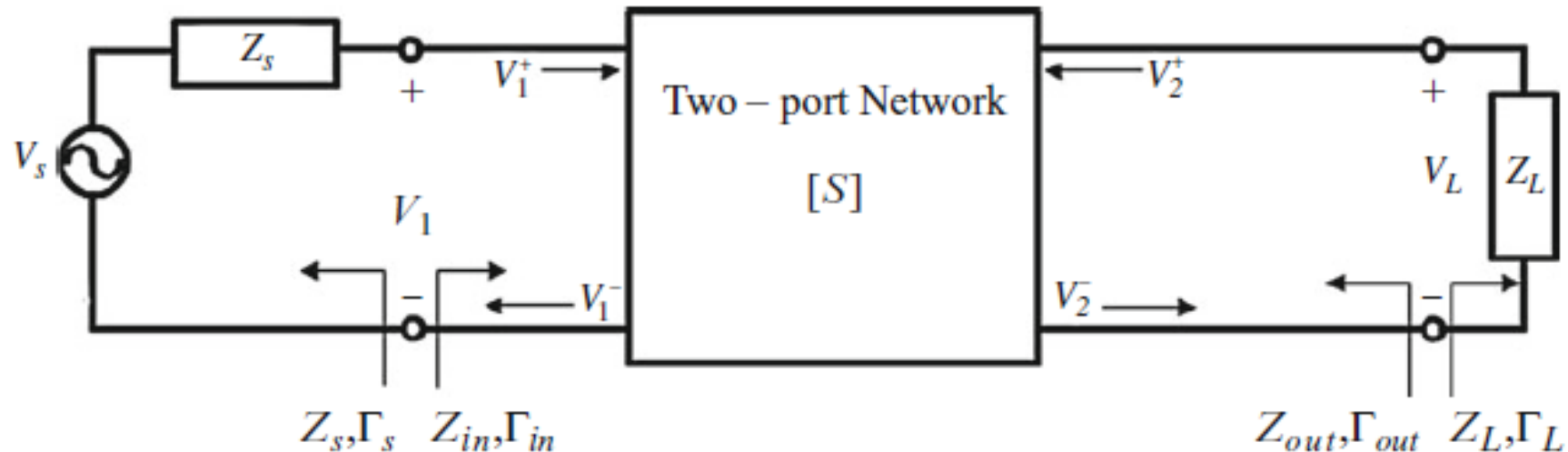

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$\Gamma_{out} = \frac{Z_{out} - Z_0}{Z_{out} + Z_0} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

$[S]$: scattering matrix of a two-port network

- Operating power gain G_P :

$$G_P = \frac{P_L}{P_{in}}$$

P_L : power delivered to the load from the two-port network

P_{in} : input power to the two-port network

- Available power gain G_A :

$$G_A = \frac{P_{avn}}{P_{avs}}$$

P_{avn} : maximum power available from network and delivered to load
(when network output is conjugate-matched)

P_{avs} : maximum power available from source and delivered to network input
(when network input is conjugate-matched)

- Transducer power gain G_T :

$$G_T = \frac{P_L}{P_{avs}}$$

- When input and output are conjugate-matched:

$$G_P = G_A = G_T$$

- Operating power gain G_P : source & load not matched
- Available power gain G_A : source & load matched
- Transducer power gain G_T : source matched, load not matched

$$\boxed{G_P \leq G_T \leq G_A}$$

- For conjugate-match at input and output:

$$G_P = G_T = G_A$$

- Gain in dB:

$$G \text{ (dB)} = 10\log_{10}G$$

- Two-port network power gains

$$P_{in} = \frac{1}{2Z_0} |V_1^+|^2 (1 - |\Gamma_{in}|^2) = \frac{|V_S|^2}{8Z_0} \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2), \text{ (power input at port 1)}$$

$$P_L = \frac{|V_1^+|^2}{2Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22} \Gamma_L|^2} = \frac{|V_S|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_L|^2) |1 - \Gamma_S|^2}{|1 - S_{22} \Gamma_L|^2 |1 - \Gamma_S \Gamma_{in}|^2} \text{ (power input at load)}$$

$$\max(P_{in}) = P_{avs}$$

$$P_{in} : \text{maximum if } \Gamma_{in} = \Gamma_S^* \text{ or } Z_{in} = Z_S^*$$



$$P_{avs} = P_{in} \Big|_{\Gamma_{in} = \Gamma_S^*} = \frac{|V_S|^2}{8Z_0} \frac{|1 - \Gamma_S|^2}{(1 - |\Gamma_S|^2)}$$

$$\max(P_L) = P_{avn}$$

$$P_L : \text{maximum if } \Gamma_L = \Gamma_{out}^* \text{ or } Z_L = Z_{out}^*$$



$$P_{avn} = \frac{|V_S|^2}{8Z_0} |S_{21}|^2 \frac{|1 - \Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2 (1 - |\Gamma_{out}|^2)}$$

Similarly, the power available from the network, P_{avn} , is the maximum power that can be delivered to the load. Thus, from (12.7),

$$P_{\text{avn}} = P_L \bigg|_{\Gamma_L = \Gamma_{\text{out}}^*} = \frac{|V_S|^2 |S_{21}|^2 (1 - |\Gamma_{\text{out}}|^2) |1 - \Gamma_S|^2}{8Z_0 |1 - S_{22}\Gamma_{\text{out}}^*|^2 |1 - \Gamma_S\Gamma_{\text{in}}|^2} \bigg|_{\Gamma_L = \Gamma_{\text{out}}^*}. \quad (12.10)$$

In (12.10), Γ_{in} must be evaluated for $\Gamma_L = \Gamma_{\text{out}}^*$. From (12.3a), it can be shown that

$$|1 - \Gamma_S\Gamma_{\text{in}}|^2 \bigg|_{\Gamma_L = \Gamma_{\text{out}}^*} = \frac{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{\text{out}}|^2)^2}{|1 - S_{22}\Gamma_{\text{out}}^*|^2},$$

which reduces (12.10) to

$$P_{\text{avn}} = \frac{|V_S|^2}{8Z_0} \frac{|S_{21}|^2 |1 - \Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{\text{out}}|^2)}. \quad (12.11)$$

$$G_P = \frac{P_L}{P_{in}} = \frac{(1-|\Gamma_L|^2)|S_{21}|^2}{|1-S_{22}\Gamma_L|^2(1-|\Gamma_{in}|^2)} : \text{operating gain}$$

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{(1-|\Gamma_S|^2)|S_{21}|^2}{|1-S_{11}\Gamma_S|^2(1-|\Gamma_{out}|^2)} : \text{available gain}$$

$$G_T = \frac{P_L}{P_{avs}} = \frac{(1-|\Gamma_S|^2)(1-|\Gamma_L|^2)|S_{21}|^2}{|(1-S_{11}\Gamma_S)(1-S_{22}\Gamma_L)-S_{12}S_{21}\Gamma_S\Gamma_L|^2} : \text{transducer gain}$$

$$G_T = \frac{1-|\Gamma_S|^2}{|1-\Gamma_{in}\Gamma_S|^2}|S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2} = \frac{1-|\Gamma_S|^2}{|1-\Gamma_{11}\Gamma_S|^2}|S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-\Gamma_{out}\Gamma_L|^2}$$

$$G_{mag} = \frac{|S_{21}|}{|S_{12}|} \left(K - \sqrt{K^2 - 1} \right) : \text{maximum available gain } (K > 1)$$

$$G_{msg} = \frac{|S_{21}|}{|S_{12}|} : \text{maximum stable gain } (K = 1)$$

$$K = \frac{1-|S_{11}|^2-|S_{22}|^2+|\Delta|^2}{2|S_{12}S_{21}|}$$

$$\Gamma_L = \Gamma_S = 0, \quad \longrightarrow \quad G_T = |S_{21}|^2.$$

$$\Gamma_{\text{in}} = S_{11} \text{ when } S_{12} = 0$$

$$G_{TU} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|1 - S_{11}\Gamma_S|^2 |1 - S_{22}\Gamma_L|^2}. \quad (\text{Unilateral transducer gain})$$

$$G_{TU} = G_S |S_{21}|^2 G_L$$

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} \quad (\text{source-match gain})$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} \quad (\text{load-match gain})$$

$$M_{\text{in}} = \frac{P_{\text{in}}}{P_{\text{avs}}} = 1 - \left| \frac{\Gamma_{\text{in}} - \Gamma_S^*}{1 - \Gamma_{\text{in}}\Gamma_S} \right|^2 \quad (\text{source mismatch factor})$$

$$M_{\text{out}} = \frac{P_L}{P_{\text{avn}}} = 1 - \left| \frac{\Gamma_{\text{out}} - \Gamma_L^*}{1 - \Gamma_{\text{out}}\Gamma_L} \right|^2 \quad (\text{load mismatch factor})$$

■ Example

A silicon bipolar junction transistor has the following scattering parameters at 1.0 GHz, with a $50\ \Omega$ reference impedance:

$$S_{11} = 0.38\angle -158^\circ$$

$$S_{12} = 0.11\angle 54^\circ$$

$$S_{21} = 3.50\angle 80^\circ$$

$$S_{22} = 0.40\angle -43^\circ$$

The source impedance is $Z_S = 25\ \Omega$ and the load impedance is $Z_L = 40\ \Omega$. Compute the power gain, the available power gain, and the transducer power gain.

$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} = \frac{25 - 50}{25 + 50} = -0.333,$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{40 - 50}{40 + 50} = -0.111.$$

$$\Gamma_{\text{in}} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.365 \angle -152^\circ,$$

$$\Gamma_{\text{out}} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = 0.545 \angle -43^\circ.$$


$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{\text{in}}|^2) |1 - S_{22}\Gamma_L|^2} = 13.1.$$

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{\text{out}}|^2)} = 19.8.$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_S\Gamma_{\text{in}}|^2 |1 - S_{22}\Gamma_L|^2} = 12.6.$$

■ Input and output matching of two-port networks

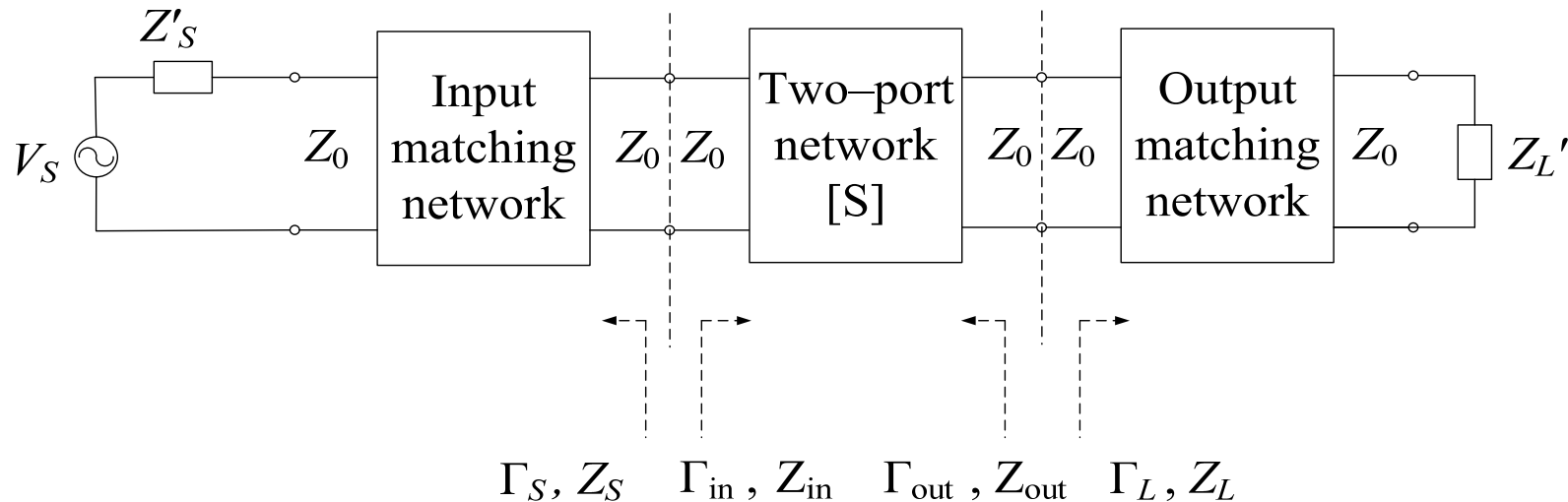- Input and output simultaneous conjugate matching: solution to (1) and (2)



$$Z_{in} = Z_S^* \rightarrow \Gamma_{in} = \Gamma_S^* \text{ if } Z_0 \text{ is real.}$$

$$Z_{out} = Z_L^* \rightarrow \Gamma_{out} = \Gamma_L^* \text{ if } Z_0 \text{ is real.}$$

- Simultaneous conjugate matching:

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \Gamma_S^* \text{ and } \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = \Gamma_L^*$$

- Input and output matching of two-port networks

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$\Delta = \det(S) = S_{11}S_{22} - S_{12}S_{21}$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} : \text{Rollett stability factor}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - S_{22}^* \Delta, \quad D_1 = |S_{11}|^2 - |\Delta|^2$$

$$C_2 = S_{22} - S_{11}^* \Delta, \quad D_2 = |S_{22}|^2 - |\Delta|^2$$

$$\boxed{\begin{aligned} Z_S &= \frac{1 + \Gamma_S}{1 - \Gamma_S} Z_0 \\ Z_L &= \frac{1 + \Gamma_L}{1 - \Gamma_L} Z_0 \end{aligned}}$$

Input matching network: $Z'_S \rightarrow Z_S$

Output matching network: $Z'_L \rightarrow Z_L$

$K \geq 1$ (necessary and sufficient condition for simultaneous matching)

$$M_{\text{in}} = 1 \text{ and } M_{\text{out}} = 1$$

$$G_P = G_T = G_A = G_{\text{MAG}} \text{ (maximum available gain)}$$

$$G_{\text{MAG}} = \frac{|S_{21}|}{|S_{12}|} \left(K - \sqrt{K^2 - 1} \right)$$

$$G_{\text{MAG}} \leq G_{\text{MSG}} = \frac{|S_{21}|}{|S_{12}|} \text{ (maximum stable gain) } (K = 1)$$

- Simultaneous conjugate matching for the unilateral case:

$$S_{12} = 0$$

$$\Gamma_S = \Gamma_{\text{in}}^* = S_{11}^* \quad \text{and} \quad \Gamma_L = \Gamma_{\text{out}}^* = S_{22}^*$$

■ Example

- With $Z_0 = Z_S = Z_L = 50 \Omega$

S-Parameters	Real	Imaginary
S_{11}	0.599858625	-0.53991373
S_{21}	-0.219423779	1.14183461
S_{12}	0.067523223	0.03730980
S_{22}	0.116580879	-0.40044436

Γ and Z	Values
Γ_{in}	$0.577503798 - j0.577166827$
Γ_{out}	$-0.096502369 - j0.402419084$
Γ_G	$0.577503798 + j0.577166827$
Γ_L	$-0.096502369 + j0.402419084$
Z_{in}	$32.57933879 - j112.810612 \Omega$
Z_{out}	$30.37350084 - j29.4972738 \Omega$
Z_G	$32.57933879 + j112.810612 \Omega$
Z_L	$30.37350084 + j29.4972738 \Omega$

- Stability: two-port network's immunity to unwanted spurious oscillation
- Unconditional stability:
 - Two-port stable for all passive source and load impedances
 - Unconditionally stable two-port network:

If $|\Gamma_{\text{in}}| \leq 1$ and $|\Gamma_{\text{out}}| \leq 1$ for all passive loads ($|\Gamma_S| \leq 1$ and $|\Gamma_L| \leq 1$)
- Conditional stability:
 - Two-port stable for a range of source and load impedances

- Stability criteria

- Rollet stability factor:

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} > 1 \quad \text{and} \quad |\Delta| < 1 \rightarrow \text{unconditionally stable}$$

Otherwise $\rightarrow$ conditionally stable

$$\Delta = \det[S] = S_{11}S_{22} - S_{12}S_{21}$$

- Edwards-Sinsky stability parameters:

$$\mu_1 = \frac{1 - |S_{11}|^2}{|S_{22} - S_{11}^* \Delta| + |S_{12}S_{21}|} > 1 \quad (\text{unconditionally stable}): \text{load stability}$$

$$\mu_1 \leq 1 \quad (\text{conditionally stable})$$

$$\mu_2 = \frac{1 - |S_{22}|^2}{|S_{11} - S_{22}^* \Delta| + |S_{12}S_{21}|} > 1 \quad (\text{unconditionally stable}): \text{source stability}$$

$$\mu_2 \leq 1 \quad (\text{conditionally stable})$$

- Relative measure of stability
 - Rollett's K -factor: does not provide
 - Edwards-Sinsky μ -factor: does provide

- Load stability region

$$|\Gamma_L - c_L| > r_L \text{ if } D_2 > 0$$

$$|\Gamma_L - c_L| < r_L \text{ if } D_2 < 0$$

- Source stability region

$$|\Gamma_S - c_S| > r_S \text{ if } D_1 > 0$$

$$|\Gamma_S - c_S| < r_S \text{ if } D_1 < 0$$

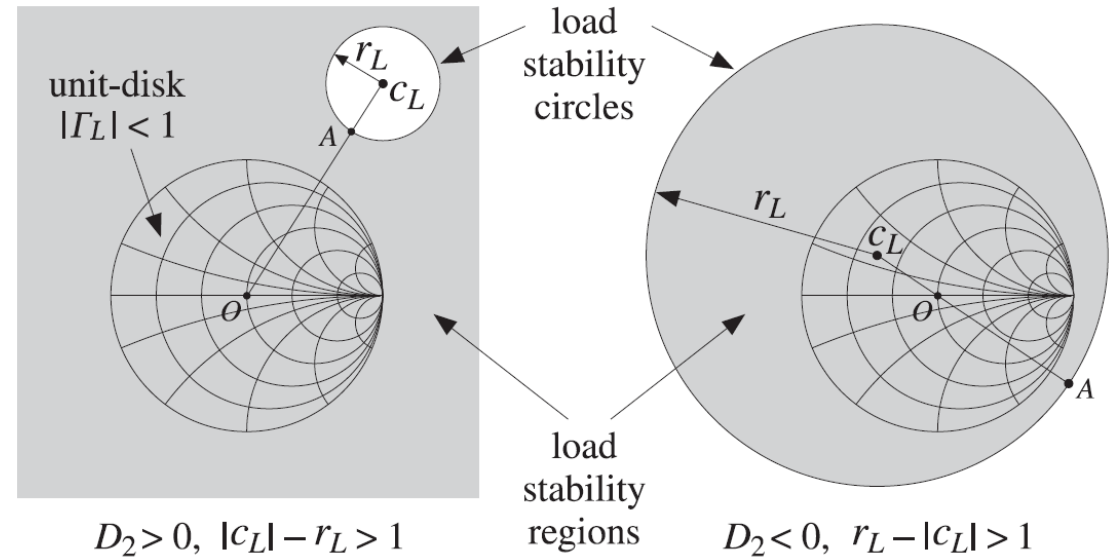


Figure: Load stability regions in the unconditionally stable case [Orfandis]

$$c_L = (S_{22}^* - S_{11}\Delta^*) / (|S_{22}|^2 - |\Delta|^2), r_L = |S_{12}S_{21}| / (|S_{22}|^2 - |\Delta|^2)$$

$$c_S = (S_{11}^* - S_{22}\Delta^*) / (|S_{11}|^2 - |\Delta|^2), r_L = |S_{12}S_{21}| / (|S_{11}|^2 - |\Delta|^2)$$

$$\Delta = \det[S] = S_{11}S_{22} - S_{12}S_{21}$$

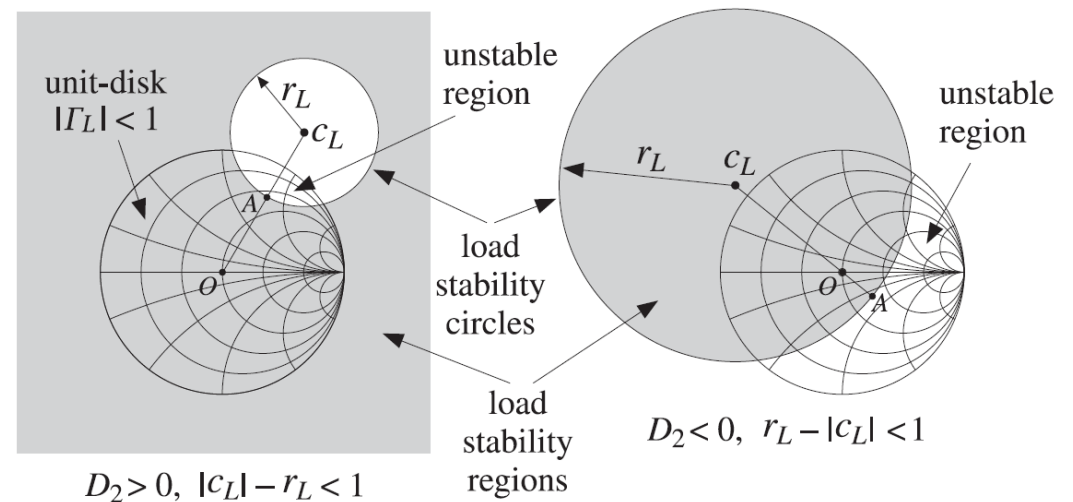


Figure: Load stability regions in the potentially unstable case [Orfandis]

6. Coding Example

■ Two-port network input & output matching

- Input data:

System reference impedance Z_0 (Ω) (real)

Source impedance Z_S' (Ω) in real/imaginary form

Load impedance Z_L' (Ω) in real/imaginary form

Two-port scattering parameters S_{11} , S_{21} , S_{12} , S_{22} in polar or rectangular form

- Output results:

A) Check stability

Calculate Rollett stability factor K and $|\Delta|$ (for unconditional stability $K > 1$ and $|\Delta| < 1$)

Calculate Edwards-Sinsky stability parameters μ_1 and μ_2 (for unconditional stability $\mu_1 > 1$ or $\mu_2 > 1$)

B) Unmatched case

Power gain G in natural unit

Available power gain G_A in natural unit

Transducer power gain G_T in natural unit

C) Matched case

Check if a conjugate-matching is possible at the input of the two-port network.

If possible, find the transformed source impedance Z_S .

Check if a conjugate-matching is possible at the output of the two-port network.

If possible, find the transformed source impedance Z_L .

Power gain G in natural unit

Available power gain G_A in natural unit

Transducer power gain G_T in natural unit

- Python code

```
# MW-05-Python-Ex1
```

```
# Two-port network input & output matching
```

```
# Input data:
```

```
# System reference impedance  $z_0$ 
```

```
# Source impedance ( $z_s'$ ), load impedance ( $z_L'$ ) in real/imaginary format
```

```
# Scattering parameters ( $s_{11}$ ,  $s_{21}$ ,  $s_{12}$ ,  $s_{22}$ ) in polar form (magnitude in natural unit, phase in degrees)
```

```
# or in rectangular form
```

```
# Output results:
```

```
# A) Check stability of two-port
```

```
# Calculate  $k$  and  $\Delta$  (Rollett stability factor)
```

```
# Calculate  $\mu_1$  and  $\mu_2$  (Edwards-Sinsky stability parameters)
```

```
# B) Unmatched case
```

```
# Power gain  $g$ , available power gain  $g_a$ , transducer power gain  $g_t$ 
```

```
# C) Matched case
```

```
# Transformed source impedance  $z_s$  in ohms
```

```
# Transformed load impedance  $z_L$  in ohms
```

```
# Power gain  $g$ , available power gain  $g_a$ , transducer power gain  $g_t$ 
```

```

import math
import cmath
rad=3.141593/180
while True:
    z0=float(input('System reference impedance Z0 (ohm, real)='))
    rsp,xsp=map(float,input('Source impedance Zs=Rs+jXs (ohm): Rs, Xs=').split())
    zsp=complex(rsp,xsp)
    rLp,xLp=map(float,input('Load impedance ZL=RL+jXL (ohm): RL, XL=').split())
    zLp=complex(rLp,xLp)
    ipolar=int(input('S-parameter form(1:polar, 2:real/imaginary)='))
    if ipolar == 1:
        s11m,s11p=map(float,input('Mag(S11), phase(S11)(deg)=').split())
        s12m,s12p=map(float,input('Mag(S12), phase(S12)(deg)=').split())
        s21m,s21p=map(float,input('Mag(S21), phase(S21)(deg)=').split())
        s22m,s22p=map(float,input('Mag(S22), phase(S22)(deg)=').split())
        s11=cmath.rect(s11m,s11p*rad)
        s12=cmath.rect(s12m,s12p*rad)
        s21=cmath.rect(s21m,s21p*rad)
        s22=cmath.rect(s22m,s22p*rad)
    elif ipolar == 2:
        s11r,s11i=map(float,input('Re(S11), Im(S11)=').split())
        s12r,s12i=map(float,input('Re(S12), Im(S12)=').split())
        s21r,s21i=map(float,input('Re(S21), Im(S21)=').split())
        s22r,s22i=map(float,input('Re(S22), Im(S22)=').split())
        s11=complex(s11r,s11i)
        s12=complex(s12r,s12i)
        s21=complex(s21r,s21i)
        s22=complex(s22r,s22i)

```

```

# STABILITY FACTOR:
print(' ')
d=s11*s22-s12*s21
k=(1-abs(s11)**2-abs(s22)**2+abs(d)**2)/(2*abs(s12*s21))
mu1=(1-abs(s11)**2)/(abs(s22-d*s11.conjugate())+abs(s12*s21)) # Edward stability factor
mu2=(1-abs(s22)**2)/(abs(s11-d*s22.conjugate())+abs(s12*s21)) # Edward stability factor
print('Rollett Stability factor: K, abs(det)=' ,k,abs(d))
print('Edwards-Sinsky stability factor: mu1, mu2=' ,mu1,mu2)
# BEFORE MATCHING:
# Reflection coefficient
R_s=(zsp-z0)/(zsp+z0) # Source reflection coefficient
R_L=(zLp-z0)/(zLp+z0) # Load reflection coefficient
R_in=s11+s12*s21*R_L/(1-s22*R_L) # Input reflection looking into port 1 of the two-port network
R_out=s22+s12*s21*R_s/(1-s11*R_s) # Output reflection looking into port 2 of the two-port network
# Power gain
gp=abs(s21)**2*(1-abs(R_L)**2)/(abs(1-s22*R_L)**2*(1-abs(R_in)**2)) # power gain
ga=abs(s21)**2*(1-abs(R_s)**2)/(abs(1-s11*R_s)**2*(1-abs(R_out)**2)) # available power gain
gt=abs(s21)**2*(1-abs(R_s)**2)*(1-abs(R_L)**2)/(abs(1-s22*R_L)**2*abs(1-R_s*R_in)**2)
print('POWER GAIN BEFORE MATCHING:')
print(' Operating power gain  Gp=',gp)
print(' Available power gain  Ga=',ga)
print(' Transducer power gain Gt=',gt)
# AFTER CONJUGATE-MATCHING:
print('POWER GAIN AFTER MATCHING')
b1=1+abs(s11)**2-abs(s22)**2-abs(d)**2
b2=1+abs(s22)**2-abs(s11)**2-abs(d)**2
c1=s11-d*s22.conjugate() # complex class conjugate function
c2=s22-d*s11.conjugate()

```



```

# Check if the input side can be matched.
ds=b1**2-4*abs(c1)**2
if ds > 0:
    R_s=(b1-math.sqrt(ds))/(2*c1) # Transformed source reflection coefficient
    print(' Source side can be conjugate-matched.')
    zs=(1+R_s)*z0/(1-R_s)
    print(' Transformed source impedance: Zg=',zs)
else:
    print(' Source side cannot be conjugate-matched.')
    print(' Source impedance remains unchanged.')
# Check if the output side can be matched.
dL=b2**2-4*abs(c2)**2
if dL > 0:
    R_L=(b2-math.sqrt(dL))/(2*c2) # Transformed load reflection coefficient
    print(' Load side can be conjugate-matched.')
    zL=(1+R_L)*z0/(1-R_L)
    print(' Transformed load impedance: ZL=',zL)
else:
    print(' Load side can be conjugate-matched.')
    print(' Load impedance remains unchanged.')
# Reflecton coefficient
R_in=s11+s12*s21*R_L/(1-s22*R_L) # Input reflection looking into port 1 of the two-port network
R_out=s22+s12*s21*R_s/(1-s11*R_s) # Output reflection looking into port 2 of the two-port network

```

```

# Power gain
gp=abs(s21)**2*(1-abs(R_L)**2)/(abs(1-s22*R_L)**2*(1-abs(R_in)**2)) # power gain
ga=abs(s21)**2*(1-abs(R_s)**2)/(abs(1-s11*R_s)**2*(1-abs(R_out)**2)) # available power gain
gt= abs(s21)**2*(1-abs(R_s)**2)*(1-abs(R_L)**2)/(abs(1-s22*R_L)**2*abs(1-R_s*R_in)**2)
print(' Operating Power gain Gp=',gp)
print(' Available power gain Ga=',ga)
print(' Transducer power gain Gt=',gt)
print(' ')

```

■ Code Execution:

System reference impedance Z_0 (ohm, real)=
50

Source impedance $Z_s=R_s+jX_s$ (ohm): R_s , X_s =
20 -30

Load impedance $Z_L=R_L+jX_L$ (ohm): R_L , X_L =
200 1000

S-parameter form(1:polar, 2:real/imaginary)=
2

$\text{Re}(S_{11})$, $\text{Im}(S_{11})$ =
0.60 -0.54

$\text{Re}(S_{12})$, $\text{Im}(S_{12})$ =
0.068 0.037

$\text{Re}(S_{21})$, $\text{Im}(S_{21})$ =
-0.22 1.14

$\text{Re}(S_{22})$, $\text{Im}(S_{22})$ =
0.12 -0.40

Rollett Stability factor: K , $\text{abs}(\det)$ = 1.788787019817944 0.3841293167671533

Edwards-Sinsky stability factor: μ_1 , μ_2 = 1.5700180443335303 1.1138680355350339

POWER GAIN BEFORE MATCHING:

Operating power gain G_p = 0.12422985810190754

Available power gain G_a = 0.5637991381007336

Transducer power gain G_t = 0.021884922225449903

POWER GAIN AFTER MATCHING

Source side can be conjugate-matched.

Transformed source impedance: $Z_g = (32.66202172271324 + j112.79263043640468)$

Load side can be conjugate-matched.

Transformed load impedance: $Z_L = (30.63645680478217 + j29.551735448459848)$

Operating Power gain $G_p = 4.5837059513206855$

Available power gain $G_a = 4.583705951320686$

Transducer power gain $G_t = 4.5837059513206855$

System reference impedance Z_0 (ohm, real)=

50

Source impedance $Z_s = R_s + jX_s$ (ohm): $R_s, X_s =$

20 -30

Load impedance $Z_L = R_L + jX_L$ (ohm): $R_L, X_L =$

200 1000

S-parameter form(1:polar, 2:real/imaginary)=

1

$\text{Mag}(S_{11}), \text{phase}(S_{11})(\text{deg}) =$

0.81 -42

$\text{Mag}(S_{12}), \text{phase}(S_{12})(\text{deg}) =$

0.077 -28.6

$\text{Mag}(S_{21}), \text{phase}(S_{21})(\text{deg}) =$

1.16 100.9

$\text{Mag}(S_{22}), \text{phase}(S_{22})(\text{deg}) =$

0.42 -73.3

Rollett Stability factor: K , $\text{abs}(\det)= 1.9673844975622021 \ 0.428898084216416$

Edwards-Sinsky stability factor: $\mu_1, \mu_2= 2.1140811103219113 \ 1.1450487524927206$

POWER GAIN BEFORE MATCHING:

Operating power gain $G_p= 0.16881040993356675$

Available power gain $G_a= 0.5791607049162761$

Transducer power gain $G_t= 0.02080648614906544$

POWER GAIN AFTER MATCHING

Source side can be conjugate-matched.

Transformed source impedance: $Z_g= (41.33371075888385+116.13301647188283j)$

Load side can be conjugate-matched.

Transformed load impedance: $Z_L= (48.36785317487852+23.141966365978412j)$

Operating Power gain $G_p= 4.114225752357467$

Available power gain $G_a= 4.1142257523574655$

Transducer power gain $G_t= 4.1142257523574655$

System reference impedance Z_0 (ohm, real)=** Process Stopped **

Press Enter to exit terminal

Fin
(End)